



# Verilog-HDL

---

Reference: [Verilog HDL: a guide to digital design and synthesis, Palnitkar, Samir](#)


Some of slides in this lecture are supported by Prof. An-Yeu Wu, E.E., NTU.

# OUTLINE

---

- Introduction
  - Basics of the Verilog Language
  - Gate-level modeling
  - Data-flow modeling
  - Behavioral modeling
  - Task and function
-

# Design Methodology

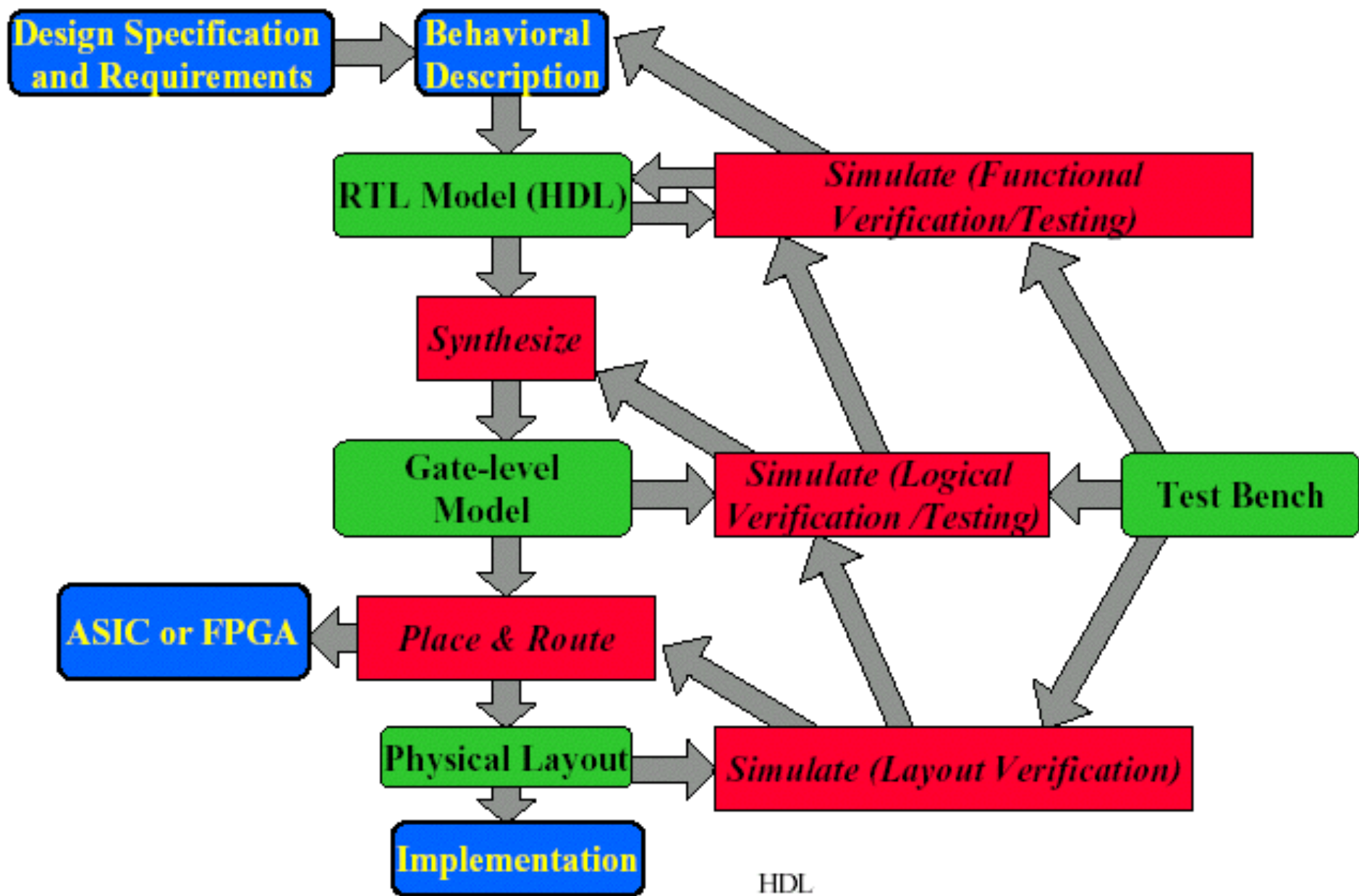

# What is Verilog HDL ?

- Mixed level modeling
  - Behavioral
    - Algorithmic ( like high level language)
    - Register transfer (Synthesizable)
  - Structural
    - Gate (AND, OR .....
    - Switch (PMOS, NOMS, JFET .....
- Single language for design and simulation
- Built-in primitives and logic functions
- User-defined primitives
- Built-in data types
- High-level programming constructs


# Basic Conventions

---

- Verilog is case sensitive
    - Keywords are in lowercase
  - Extra white space is ignored
    - But whitespace does separate tokens
  - Comments
    - One liners are //
    - Multiple lines /\* \*/
    - Comments may not be nested
-
 
# Basic unit --Module

```
module module_name (port_name);  
    port declaration  
    data type declaration  
    module functionality or structure  
endmodule
```



# D-FlipFlop

---

```
module D_FF(q,d,clk,reset);
output q;           //port declaration
input d,clk,reset; // data type declaration
reg q;
always @ (posedge reset or negedge clk)
if (reset)
    q=1'b0;
else
    q=d;
endmodule
```

---



# Instance

---

- A module provides a template which you can create actual objects.
  - When a module is invoked, Verilog creates a unique object from the template
  - The process of creating a object from module template is called instantiation
  - The object is called instance
-



# Instances

```
module adder (in1,in2,cin,sum,cout);  
.....  
endmodule
```

```
module adder8(....) ;  
adder add1(a,b,1'b0,s1,c1) ,  
      add2(.in1(a2),.in2(b2),.cin(c1),.sum(s2)  
          ,.cout(c2)) ;  
.....  
endmodule
```

Mapping port positions

Mapping names

# T-FlipFlop

---

```
module T_FF(q,clk,reset);  
output q;  
input clk,reset;  
wire d;  
D_FF dff0(q,d,clk,reset); // create an instance  
not n1(d,q);  
endmodule
```

---

# Identifier & Keywords

---


- Identifier

- User-provided names for Verilog objects in the descriptions
- Legal characters are “a-z”, “A-Z”, “0-9”, “\_”, and “\$”
- First character has to be a letter or an “\_”
  - Example: Count, \_R2D2, FIVE\$

- Keywords

- Predefined identifiers to define the language constructs
  - All keywords are defined in lower case
  - Cannot be used as identifiers
    - Example: initial, assign, module, always....
-

# Hierarchical Modeling Concepts

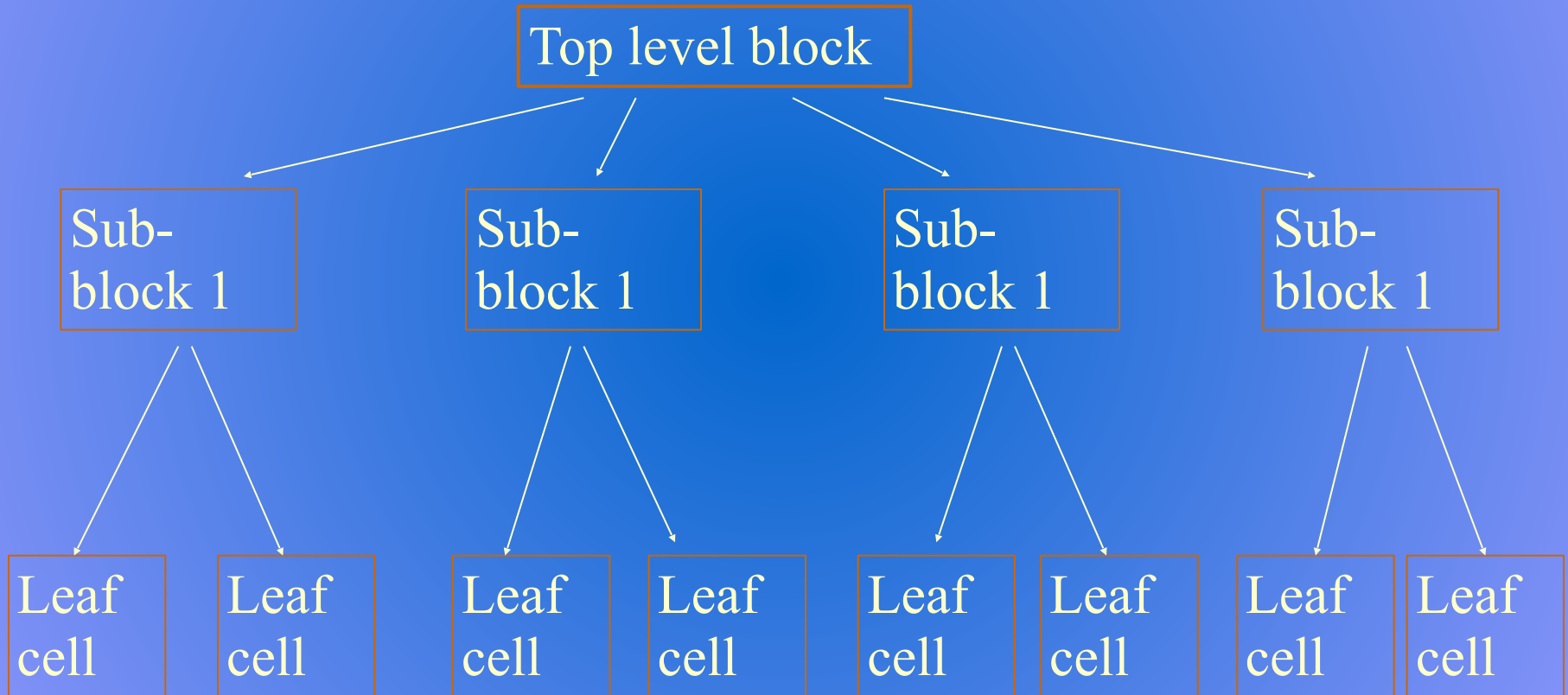


# Hierarchical Modeling Concepts

---

- Module ripple\_carry\_counter(q,clk, reset);
  - Output [3:0] q;
  - Input clk, reset;
  - T\_FF tff0(q[0], clk, reset);
  - T\_FF tff1(q[1], q[0], reset);
  - T\_FF tff0(q[2], q[1], reset);
  - T\_FF tff0(q[3], q[2], reset);
  - endmodule
-
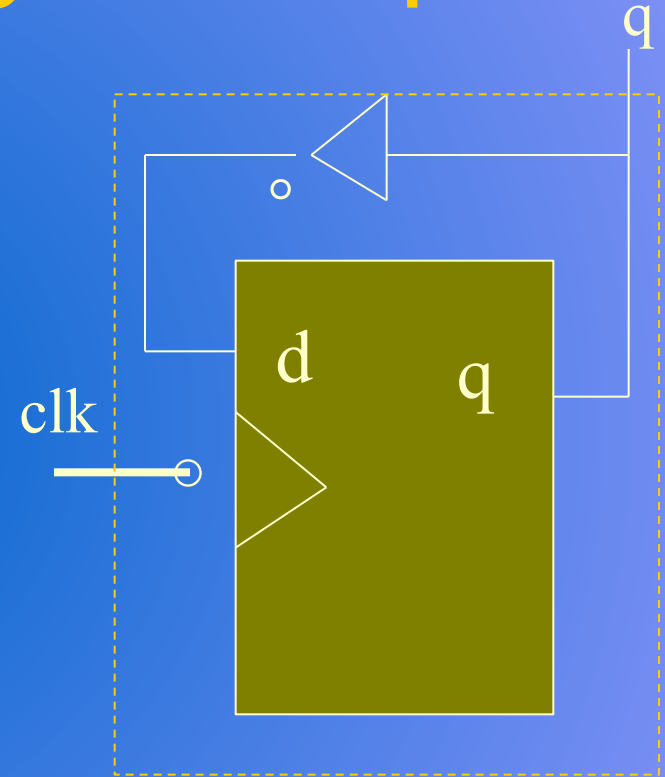
# Hierarchical Modeling Concepts

- `module T_FF(q, clk, reset);`
- `output q;`
- `input clk, reset;`
- `wire d;`
- `D_FF dff0(q, d, clk, reset);`
- `not na(d, q);`
- `endmodule`



# Hierarchical Modeling Concepts

---

- `module D_FF(q, d, clk, reset);`
  - `output q;`
  - `input d, clk, reset;`
  - `reg q;`
  - `always @(posedge reset or negedge clk)`
  - `if (reset)`
  - `q=1'b0;`
  - `else`
  - `q=d;`
  - `endmodule`
-



# 4-bits Ripple Carry Counter

